

## Department of Electrical Engineering

UET, Lahore

### Digital Systems Laboratory

## Lab # 7(a)

### Decoders: Construction, Operation and Application

#### Objective:

In this lab you will:

- Verify the operation of 74LS139 Dual 2 to 4 active low output decoder digital IC.
- Construct large decoders from small decoder units.
- Implement Boolean functions using a decoder.


#### Theoretical Background:

Discrete quantities of information are represented in digital systems by binary codes. A binary code of  $n$  bits is capable of representing up to  $2^n$  distinct elements of coded information. A decoder is a combinational circuit that converts binary information from  $n$  input lines to a maximum of  $2^n$  unique output lines. If the  $n$ -bit coded information has unused combinations, the decoder may have fewer than  $2^n$  outputs. The purpose of decoder is to generate the  $2^n$  (or fewer) min terms of  $n$  input variables. Each combination of inputs will assert a unique output. For details, study the article 4.9 from 'Digital Design, with an introduction to Verilog HDL', 5<sup>th</sup> edition, by M. Morris Mano and Michael D. Ciletti
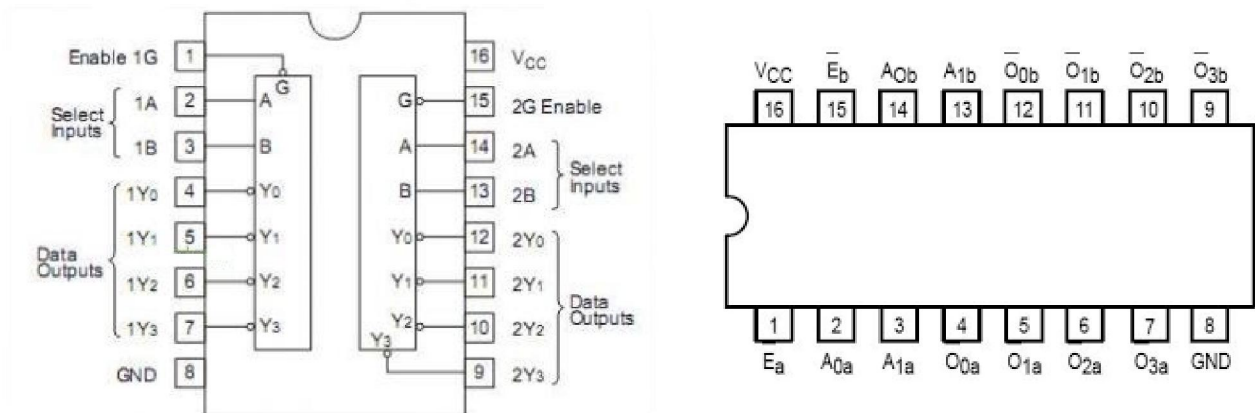
#### Apparatus:

74LS139                      Dual 2x4 active low output decoder digital IC.

The pin configuration of 74LS139 is given below:



It is an active low output IC with a pair of 2 to 4 decoders. IC chip has a 2 active low enable inputs, one for each decoder. Truth table of this IC is shown on right.

**Truth Table**

Inputs			Outputs			
$\bar{E}$	$A_0$	$A_1$	$\bar{O}_0$	$\bar{O}_1$	$\bar{O}_2$	$\bar{O}_3$
H	X	X	H	H	H	H
L	L	L	L	H	H	H
L	H	L	H	L	H	H
L	L	H	H	H	L	H
L	H	H	H	H	H	L


H = HIGH Voltage Level  
L = LOW Voltage Level  
X = Immaterial

### Lab Task (a):

Verify the operation of 74LS139 digital IC.
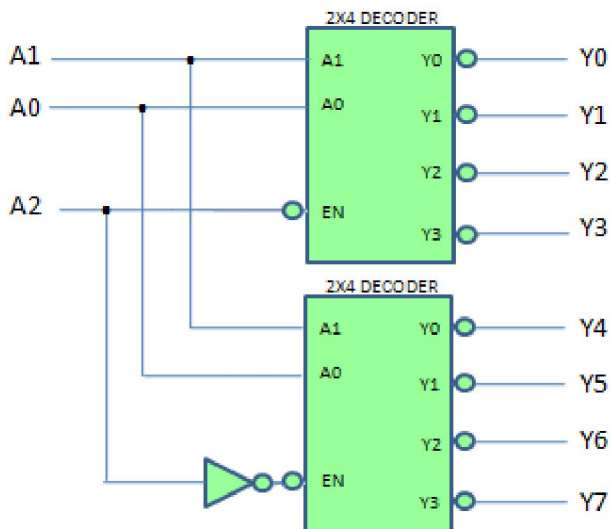
### Lab Task (b):

Construct a 3x8 decoder using two 2x4 decoders and verify its operation. Its block diagram is as follows:





Inputs			Outputs							
$A_2$	$A_1$	$A_0$	$O_0$	$O_1$	$O_2$	$O_3$	$O_4$	$O_5$	$O_6$	$O_7$
0	0	0								
0	0	1								
0	1	0								
0	1	1								
1	0	0								
1	0	1								
1	1	0								
1	1	1								
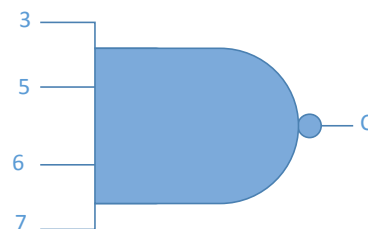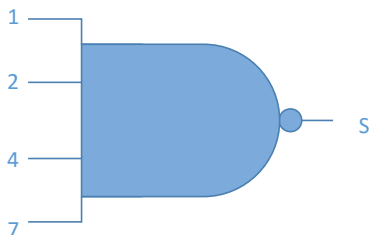
### Lab Task (c):

Implement a full adder using 3x8 decoder you made. See that outputs are active low.

$$S = \sum (1, 2, 4, 7) \quad C = \sum (3, 5, 6, 7)$$



**Comments:**

---

---

---

---

**Assignment:**

- Construct a 4x16 decoder using 2x4 decoders and verify its operation.
- Implement 2x2 multiplier using 4x16 decoder.

**Lab Instructor:** \_\_\_\_\_

**Dated:** \_\_\_\_\_